

98%

**SOUTH EASTERN UNIVERSITY OF SRI LANKA**  
**FACULTY OF ENGINEERING**

END SEMESTER EXAMINATION – JULY 2019  
SEMESTER I - 2017 / 2018

**EE 13001 - PRINCIPLES OF ELECTRICAL ENGINEERING**

Time Allowed: Three hours

Answer all six questions. All questions carry equal marks.

**Instructions:**

Answer Section A and Section B **separately** and answer script will be **collected separately**.

Please **do not** tie Section A and B together.

---

**Section A**

- 1) Consider the circuit shown in Figure Q1. All voltages are given with respect to the ground (0V).
- a) Find the voltage across the  $4\Omega$  resistor  $V_X$  and hence calculate the current through it,  $I_{(4)}$ . (20 marks)
  - b) Also find  $I_S$  by applying KCL to node B. (30 marks)
  - c) Apply KCL to node A and find  $I_I$ . (30 marks)
  - d) Calculate the power in all the resistors. (12 marks)
  - e) What is the power associated with the  $I_I$  source? (06 marks)
  - f) Indicate whether it is 'provided' or 'absorbed' by the  $I_I$  source. (02 marks)

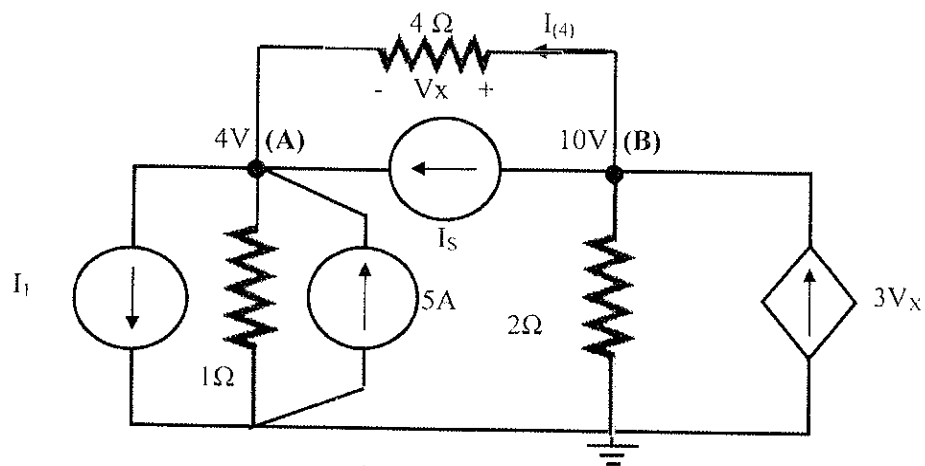


Figure Q1

- 2) Consider the circuit shown in Figure Q2.
- Simplify the circuit by combining resistors where possible. (10 marks)
  - Apply KVL to find the current through the  $30\ \Omega$  resistor. (30 marks)
  - Find the power absorbed by the  $30\ \Omega$  resistor. (20 marks)
  - What is the power associated with the dependent source? (20 marks)
  - Calculate the current through the  $10\ \Omega$  resistor. (20 marks)

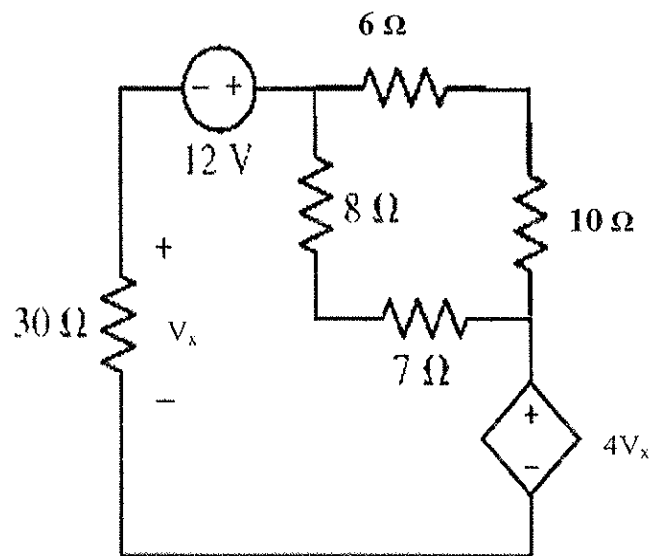


Figure Q2

- 3) a) Consider the circuit shown in Figure Q3a.
- Find the Thevenin equivalent of the circuit connected to  $R_L$ . (40 marks)
  - What value of  $R_L$  would absorb maximum power from the circuit? (10 marks)

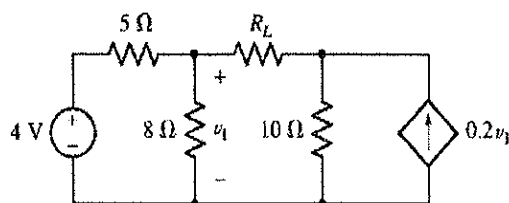


Figure Q3a

- b)
- i) A resistance  $R$  and a  $5\ \mu\text{F}$  capacitor are connected in series with a switch, across a  $200\ \text{V}$  d.c. supply. Calculate the value of  $R$  that will make the capacitor voltage reach  $100\ \text{V}$ ,  $5$  seconds after the switch has been closed. (20 marks)
  - ii) What will be the current through the resistor  $R$ ,  $10\text{s}$  after closing the switch? (30 marks)

### Section B

- 4) i) Mathematically prove the inductive impedance and the capacitive impedance, while explaining their corresponding phase angles. (20 marks)
- ii) A given RL series circuit, a voltage of  $7.9\ \text{V}$  at  $48.86\ \text{Hz}$  produces a current of  $568.45\ \text{mA}$  while the same voltage at  $68.45\ \text{Hz}$  produces  $456.89\ \text{mA}$ . What are the values of  $R$  and  $L$  in the circuit? (20 marks)
- iii) A  $65.286\ \text{Hz}$  sinusoidal voltage  $v = (156.75)\sin(\omega t)$  is applied to a series RL connection. The values of the resistance and the inductance are  $8.9\ \text{ohms}$  and  $0.0256\ \text{H}$  respectively. (Strictly state your assumptions.) (30 marks)
  - a) Calculate the r.m.s value of the current in the circuit and its phase angle with respect to the voltage.
  - b) What is the expression for the instantaneous current in the circuit.
  - c) Find the r.m.s value and the phase of the voltages appearing across the resistance and the inductance, with clear steps.
  - d) Show the variation of all the vector variables on a sinusoidal pattern, in time domain.
  - e) Calculate the average power dissipated by the circuits.
  - f) How can the power factor be of useful in the circuit, in terms of its value?
- iv) A variable capacitor is connected in series with a circuit consisting of a non-inductive resistance of  $123\ \text{ohms}$  in parallel with a coil across a  $189\ \text{V}$ ,  $58\ \text{Hz}$  supply. The coil has an inductance of  $2.53\ \text{H}$ . (30 marks)
  - (a) State the assumption that you would make at the start of the sum.

- (b) Calculate the capacitance of the capacitor, when the power factor of the circuit is unity.
- (c) Compute the corresponding potential difference across the capacitor. Draw the vector diagram, to scale, representing all the voltage and currents.
- (d) Draw the vector polygon to indicate the resultant vector.
- 5) i) Distinguish active power, apparent power and reactive power, along with their units. (10 marks)
- ii) Discuss a practical application mathematically where active power, reactive power and apparent power be used. (10 marks)
- iii) The excited voltage is 95.75V to a circuit, and is found to lag the current by  $30^\circ$  (40 marks)
- a) Comment on the nature of the power factor concerned.
- b) Compute the magnitude of the power factor, and discuss its possible variation?
- c) Deduce whether the circuit is to be either inductive or capacitive.
- d) Find the active and reactive power associated with the circuit, from first principles.
- iv) a) What is electrical resonance? And derive an expression for the resonant frequency, differentiating the serial and the parallel resonance. (40 marks)
- b) Describe the following graphically, in account of the resonant curve,
- Quality Factor / Degree of Merit  
Selectivity  
Sharpness  
Bandwidth  
Half Power Points  
Power Factor at Resonance
- c) An inductor having an inductance of 30.456 mH and resistance 8.45 ohms is connected in series with a 28.754  $\mu\text{F}$  capacitor across a 198.789 V AC supply. Thus, find numerically the resonance frequency of the system, current at resonance and the Degree of Merit. Hence or otherwise, explain the bandwidth of the said application as well.

- 6) i) (a) Distinguish RMS value, average value and the rectified average value (5 marks)  
of a wave mathematically, and also in terms of their physical significance.
- (b) Derive the expressions for the RMS and the Average values for a (5 marks)  
sinusoidal wave form.
- ii) Determine the effective value of the following waveform. (20 marks)

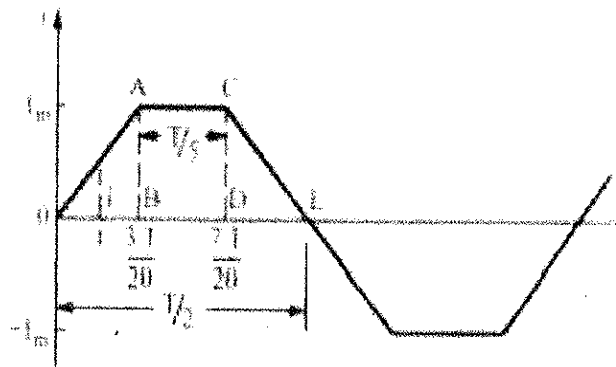


Figure Q 6.1

- iii) (20 marks)  
A delayed full-wave rectified sinusoidal current is observed with an average value of half the maximum value. Thus, find the delay angle

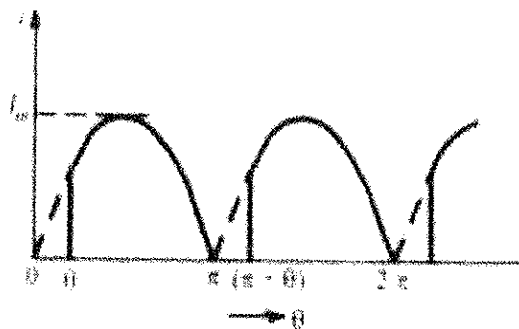


Figure Q 6.2

iv)

(50 marks)

Determine the branch voltages, currents and power delivered by the source, with respect to the given circuit below. Draw the corresponding phasor diagram to indicate all the voltage and the current variables.

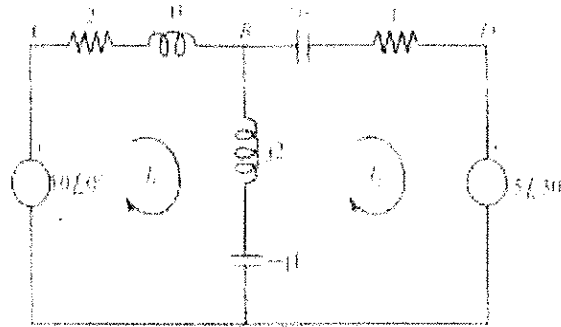


Figure 6.3